


# CSCI 463 – Midterm (Fall 2019)

Name: \_\_\_\_\_ Z-number: \_\_\_\_\_

Each question has one and only one correct answer. Choose the best possible/most accurate answer for each question.


All answers must be given in the context of the lectures and assignments used in the course.

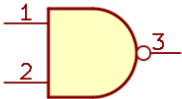1. What function does this symbol represent?




Ⓐ AND, Ⓑ NAND, Ⓒ OR, Ⓓ NOT, Ⓔ XOR

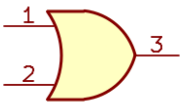2. What function does this symbol represent?




Ⓐ AND, Ⓑ NAND, Ⓒ OR, Ⓓ NOT, Ⓔ XOR

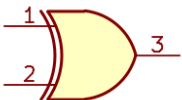3. What function does this symbol represent?




Ⓐ AND, Ⓑ NAND, Ⓒ OR, Ⓓ NOT, Ⓔ XOR

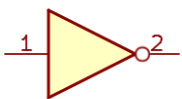4. What function does this symbol represent?




Ⓐ AND, Ⓑ NAND, Ⓒ OR, Ⓓ NOT, Ⓔ XOR

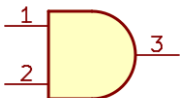5. What function does this symbol represent?




Ⓐ AND, Ⓑ NAND, Ⓒ OR, Ⓓ NOT, Ⓔ XOR

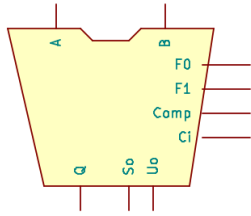6. What function does this symbol represent?




- Ⓐ D-latch, Ⓑ Demultiplexer, Ⓒ ALU, Ⓓ Multiplexer, Ⓔ Register

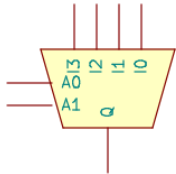7. What function does this symbol represent?




- Ⓐ D-latch, Ⓑ Demultiplexer, Ⓒ ALU, Ⓓ Multiplexer, Ⓔ Register

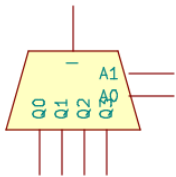8. What function does this symbol represent?




- Ⓐ D-latch, Ⓑ Demultiplexer, Ⓒ ALU, Ⓓ Multiplexer, Ⓔ Register

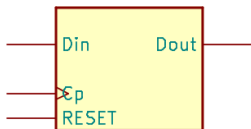9. What function does this symbol represent?




- Ⓐ D-latch, Ⓑ RS-latch, Ⓒ ALU, Ⓓ Full Adder, Ⓔ Half adder

10. What is the following circuit?

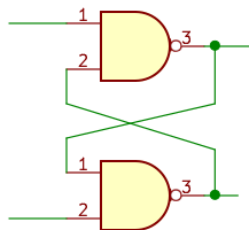


- Ⓐ D-latch, Ⓑ RS-latch, Ⓒ ALU, Ⓓ Full Adder, Ⓔ Half adder

11. What is the following circuit?

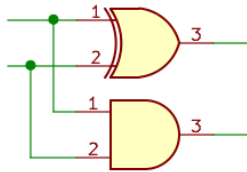


- (A) D-latch, (B) RS-latch, (C) ALU, (D) Full Adder, (E) Half adder

12. What is the following circuit?

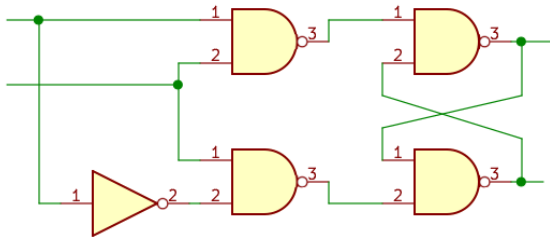

- (A) D-latch, (B) RS-latch, (C) ALU, (D) Full Adder, (E) Half adder

13. What is the following circuit?

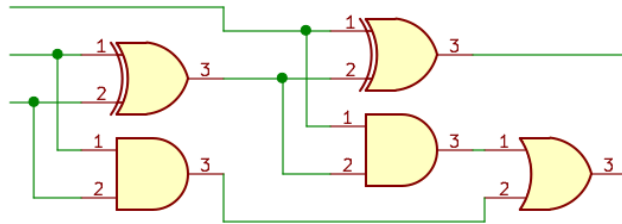

- (A) D-latch, (B) RS-latch, (C) ALU, (D) Full Adder, (E) Half adder

14. Which is the truth table for the XOR function?

(A)			(B)			(C)			(D)			(E)		
A	B	Q	A	B	Q	A	B	Q	A	B	Q	A	B	Q
1	1	1	0	0	0	0	0	1	0	0	0	0	0	0
0	1	1	0	1	1	0	1	1	0	1	1	0	1	0
1	0	1	1	0	1	1	0	1	1	0	1	1	0	0
1	1	0	1	1	1	1	1	0	1	1	0	1	1	1

15. Which is the truth table for the OR function?

(A)			(B)			(C)			(D)			(E)		
A	B	Q	A	B	Q	A	B	Q	A	B	Q	A	B	Q
1	1	1	0	0	0	0	0	1	0	0	0	0	0	0
0	1	1	0	1	1	0	1	1	0	1	1	0	1	0
1	0	1	1	0	1	1	0	1	1	0	1	1	0	0
1	1	0	1	1	1	1	1	0	1	1	0	1	1	1

16. Which is the truth table for the NAND function?

Ⓐ			Ⓑ			Ⓒ			Ⓓ			Ⓔ		
A	B	Q	A	B	Q	A	B	Q	A	B	Q	A	B	Q
1	1	1	0	0	0	0	0	1	0	0	0	0	0	0
0	1	1	0	1	1	0	1	1	0	1	1	0	1	0
1	0	1	1	0	1	1	0	1	1	0	1	1	0	0
1	1	0	1	1	1	1	1	0	1	1	0	1	1	1

17. What is the clock input used for in those circuits that have one?

- Ⓐ To tell time,
- Ⓑ To determine when to change its state,
- Ⓒ To determine when to change its input,
- Ⓓ To disable the output,
- Ⓔ To store the demultiplexer output in the ALU

18. Which is the truth table for a full-adder?

Ⓐ				Ⓑ				Ⓒ				Ⓓ				Ⓔ							
A	B	Co	S	A	B	Ci	Co	S	A	B	Ci	Co	S	A	B	Ci	Co	S	A	B	Ci	Co	S
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
0	1	0	1	0	0	1	0	0	0	0	1	0	1	0	0	1	0	1	0	0	1	1	1
1	0	0	1	0	1	0	0	0	0	1	0	0	1	0	1	0	0	1	0	1	0	1	1
1	1	1	0	0	1	1	1	0	0	1	1	1	0	0	1	1	1	0	0	1	1	0	0
				1	0	0	0	1	1	0	0	0	1	1	0	0	0	1	1	0	0	1	1
				1	0	1	1	1	1	0	1	1	0	1	1	1	1	0	1	0	1	0	0
				1	1	0	1	1	1	1	0	1	0	1	1	1	1	0	1	1	0	0	0
				1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1

19. Which is the truth table for a half-adder?

Ⓐ				Ⓑ				Ⓒ					Ⓓ					Ⓔ					
A	B	Co	S	A	B	Ci	Co	S	A	B	Ci	Co	S	A	B	Ci	Co	S	A	B	Ci	Co	S
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
0	1	0	1	0	0	1	0	0	0	0	1	0	1	0	0	1	0	1	0	0	1	1	1
1	0	0	1	0	1	0	0	0	0	1	0	0	1	0	1	0	0	1	0	1	0	1	1
1	1	1	0	0	1	1	1	0	0	1	1	1	0	0	1	1	1	0	0	1	1	0	0
				1	0	0	0	1	1	0	0	0	1	1	0	0	0	1	1	0	0	1	1
				1	0	1	1	1	1	0	1	1	0	1	1	1	1	0	1	0	1	0	0
				1	1	0	1	1	1	1	0	1	0	1	1	1	1	0	1	1	0	0	0
				1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1

20. What is the LSB of the decimal number 1234?

- Ⓐ 0, Ⓑ 1, Ⓒ 2, Ⓓ 3, Ⓔ 4

21. What is the LSB of the decimal number 123?

- Ⓐ 0, Ⓑ 1, Ⓒ 2, Ⓓ 3, Ⓔ 4

22. What do the signals labeled I0-In do on a multiplexer?

- Ⓐ Data inputs, Ⓑ Data outputs, Ⓒ Address inputs, Ⓓ Address outputs, Ⓔ Clock signals

23. What are signals labeled A0-An called on a multiplexer?

- Ⓐ Data inputs, Ⓑ Data outputs, Ⓒ Address inputs, Ⓓ Address outputs, Ⓔ Clock signals

24. What do the signals labeled A0-An do on a multiplexer?
- Ⓐ Select which output to enable,
  - Ⓑ Select which input to propagate,
  - Ⓒ Select which output to disable,
  - Ⓓ Select which input to disable,
  - Ⓔ Select which boolean function to perform
25. Which signals on a demultiplexer are its inputs?
- Ⓐ A0-An Ⓑ I0-In Ⓒ Q0-Qn Ⓓ Both A and B Ⓔ Both A and C
26. Which signals on a demultiplexer are its outputs?
- Ⓐ A0-An Ⓑ I0-In Ⓒ Q0-Qn Ⓓ Both A and B Ⓔ Both A and C
27. What do the signals labeled F0-Fn do on an ALU?
- Ⓐ Select which output to enable,
  - Ⓑ Select which input to propagate,
  - Ⓒ Select which arithmetic operation to perform,
  - Ⓓ Select which logical operation to perform,
  - Ⓔ Both C and D
28. Which circuit can add these two binary numbers: 1101 1100
- Ⓐ RS-latch, Ⓑ Demultiplexer, Ⓒ ALU, Ⓓ Full Adder, Ⓔ Half adder
29. How many full adders are needed to add two signed 8 bit numbers?
- Ⓐ 1, Ⓑ 2, Ⓒ 4, Ⓓ 8, Ⓔ 16
30. What types of clocks are used for registers?
- Ⓐ RS, Ⓑ Level, Ⓒ Edge, Ⓓ Boolean, Ⓔ GPS
31. What is an RS latch used for?
- Ⓐ To reset the ALU,
  - Ⓑ To store one bit,
  - Ⓒ To store two bits,
  - Ⓓ To generate the overflow status,
  - Ⓔ To trigger the Multiplexer
32. What is a bus?
- Ⓐ A register,
  - Ⓑ To store one bit,
  - Ⓒ To store two bits,
  - Ⓓ A collection of related signals,
  - Ⓔ A collection of unrelated signals
33. Which of the following is true?
- Ⓐ High-level-sensitive latches will retain the input present during the falling edge of the enable signal,
  - Ⓑ High-level-sensitive latches allow the output to change multiple times when the enable signal is high,
  - Ⓒ Falling-edge-triggered latches retain the input when the clock changes from 1 to 0,
  - Ⓓ All of the above
  - Ⓔ None of the above

The following waveform includes, among other things, the signals of an RS latch whose output is labeled  $Q$ :

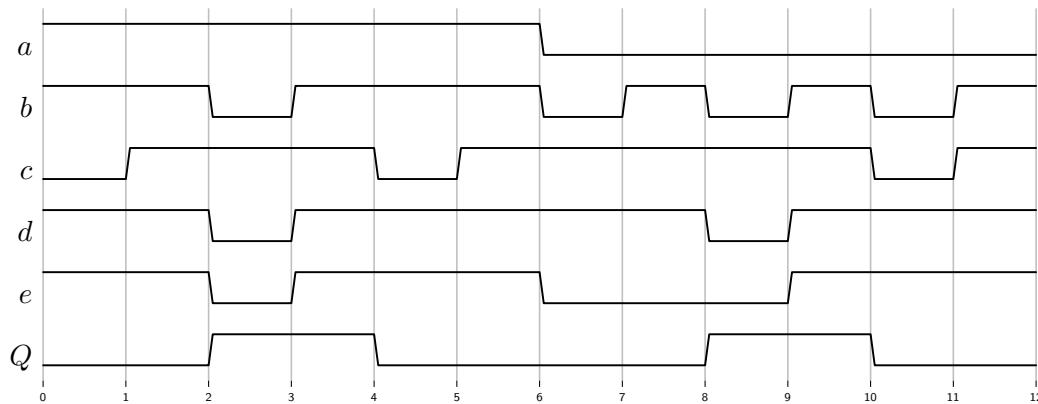


Figure 1: A Timing Diagram

34. Which signal labeled  $a-e$  in Figure 1 is the *reset* signal?
35. Which signal labeled  $a-e$  in Figure 1 is the *set* signal?
36. What does overflow mean?
  - (A) A carry out of the LSB,
  - (B) A carry into the MSB,
  - (C) An operation can not fit into the destination register,
  - (D) A logical operation has no inputs,
  - (E) A collection of related signals
37. What signifies that an *unsigned* overflow has taken place during an addition?
  - (A) A carry out of the LSB,
  - (B) A carry into the MSB,
  - (C) A carry out of the MSB,
  - (D) A carry into the LSB that is different from the carry out of the LSB,
  - (E) A carry into the MSB that is different from the carry out of the MSB
38. What signifies that a *signed* overflow has taken place during an addition?
  - (A) A carry out of the LSB,
  - (B) A carry into the MSB,
  - (C) A carry out of the MSB,
  - (D) A carry into the LSB that is different from the carry out of the LSB,
  - (E) A carry into the MSB that is different from the carry out of the MSB
39. What the hexadecimal value of the binary number 10110001?
  - (A) 69, (B) C0, (C) 19, (D) C2, (E) B1
40. What the hexadecimal value of the binary number 01101001?
  - (A) 69, (B) C0, (C) 19, (D) C2, (E) B1
41. What the binary value of the hexadecimal number 22?
  - (A) 10101010, (B) 11110000, (C) 00000000, (D) 10100101, (E) 00100010
42. What the binary value of the hexadecimal number A5?
  - (A) 10101010, (B) 11110000, (C) 00000000, (D) 10100101, (E) 00100010

Given the following schematic symbol (that matches that discussed lecture), truth table and waveform diagram (labeled such that time  $t_0$  appears at the far left edge and  $t_{16}$  appears at the right):

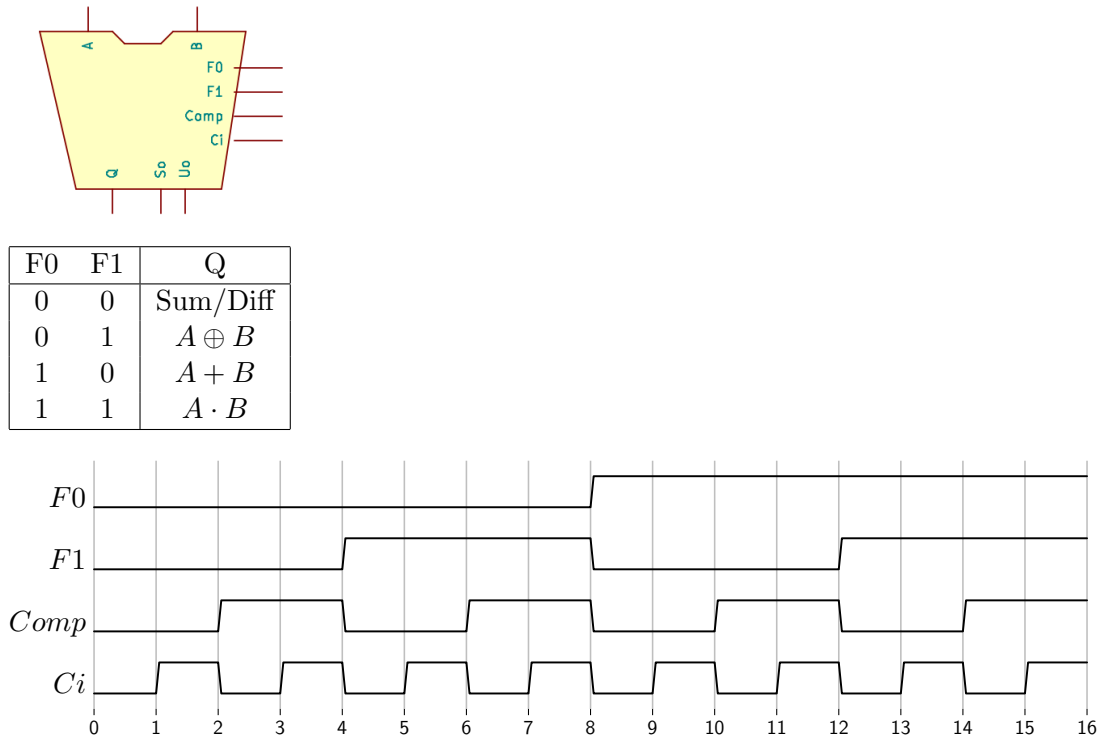


Figure 2: A Timing Diagram

43. What function is being performed between time  $t_0$  and  $t_1$ ?  
 (A) Add, (B) Subtract, (C) XOR, (D) OR, (E) AND
44. What function is being performed between time  $t_3$  and  $t_4$ ?  
 (A) Add, (B) Subtract, (C) XOR, (D) OR, (E) AND
45. What function is being performed between time  $t_4$  and  $t_5$ ?  
 (A) Add, (B) Subtract, (C) XOR, (D) OR, (E) AND
46. What function is being performed between time  $t_8$  and  $t_9$ ?  
 (A) Add, (B) Subtract, (C) XOR, (D) OR, (E) AND
47. What function is being performed between time  $t_{12}$  and  $t_{13}$ ?  
 (A) Add, (B) Subtract, (C) XOR, (D) OR, (E) AND
48. What function is being performed between time  $t_{13}$  and  $t_{14}$ ?  
 (A) Add, (B) Subtract, (C) XOR, (D) OR, (E) AND
49. What function is being performed between time  $t_5$  and  $t_6$ ?  
 (A)  $A \oplus B$ , (B)  $\bar{A} \cdot B$ , (C)  $A \cdot B$ , (D)  $A \cdot \bar{B}$ , (E)  $A + \bar{B}$
50. What function is being performed between time  $t_{14}$  and  $t_{15}$ ?  
 (A)  $A \oplus B$ , (B)  $\bar{A} \cdot B$ , (C)  $A \cdot B$ , (D)  $A \cdot \bar{B}$ , (E)  $A + \bar{B}$