


CSCI 463 – Midterm (Fall 2019)

Name: _____ Z-number: _____

Each question has one and only one correct answer. Choose the best possible/most accurate answer for each question.


All answers must be given in the context of the lectures and assignments used in the course.

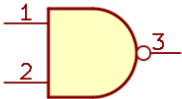1. What function does this symbol represent?




- Ⓐ AND, Ⓑ **NAND**, Ⓒ OR, Ⓓ NOT, Ⓔ XOR

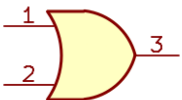2. What function does this symbol represent?




- Ⓐ AND, Ⓑ NAND, Ⓒ **OR**, Ⓓ NOT, Ⓔ XOR

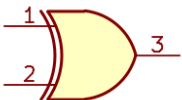3. What function does this symbol represent?




- Ⓐ AND, Ⓑ NAND, Ⓒ OR, Ⓓ NOT, Ⓔ **XOR**

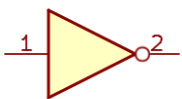4. What function does this symbol represent?




- Ⓐ AND, Ⓑ NAND, Ⓒ OR, Ⓓ **NOT**, Ⓔ XOR

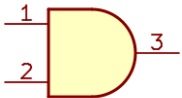5. What function does this symbol represent?




- Ⓐ **AND**, Ⓑ NAND, Ⓒ OR, Ⓓ NOT, Ⓔ XOR

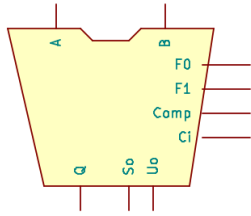6. What function does this symbol represent?




- (A) D-latch, (B) Demultiplexer, (C) ALU, (D) Multiplexer, (E) Register

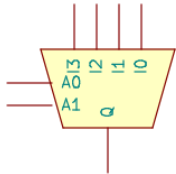7. What function does this symbol represent?




- (A) D-latch, (B) Demultiplexer, (C) ALU, (D) Multiplexer, (E) Register

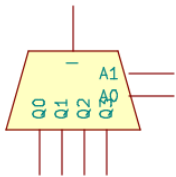8. What function does this symbol represent?




- (A) D-latch, (B) Demultiplexer, (C) ALU, (D) Multiplexer, (E) Register

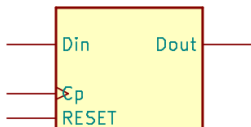9. What function does this symbol represent?




- (A) D-latch, (B) RS-latch, (C) ALU, (D) Full Adder, (E) Half adder

10. What is the following circuit?

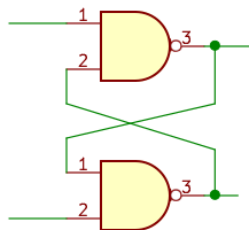


- (A) D-latch, (B) RS-latch, (C) ALU, (D) Full Adder, (E) Half adder

11. What is the following circuit?

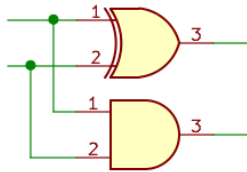


- (A) D-latch, (B) RS-latch, (C) ALU, (D) Full Adder, (E) Half adder

12. What is the following circuit?

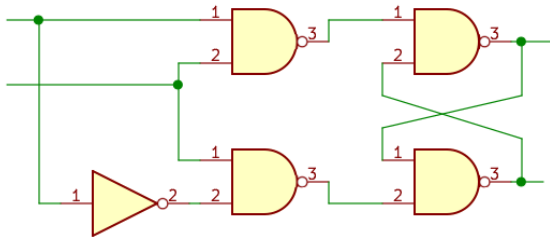

- (A) D-latch, (B) RS-latch, (C) ALU, (D) Full Adder, (E) Half adder

13. What is the following circuit?

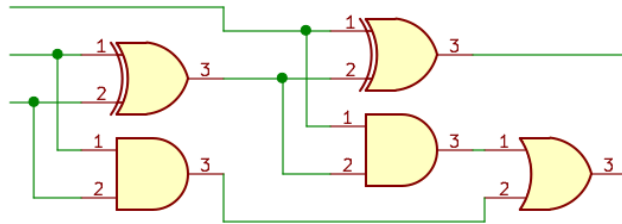

- (A) D-latch, (B) RS-latch, (C) ALU, (D) Full Adder, (E) Half adder

14. Which is the truth table for the XOR function?

(A)	(B)	(C)	(D)	(E)
A B Q	A B Q	A B Q	A B Q	A B Q
1 1 1	0 0 0	0 0 1	0 0 0	0 0 0
0 1 1	0 1 1	0 1 1	0 1 1	0 1 0
1 0 1	1 0 1	1 0 1	1 0 1	1 0 0
1 1 0	1 1 1	1 1 0	1 1 0	1 1 1

15. Which is the truth table for the OR function?

(A)	(B)	(C)	(D)	(E)
A B Q	A B Q	A B Q	A B Q	A B Q
1 1 1	0 0 0	0 0 1	0 0 0	0 0 0
0 1 1	0 1 1	0 1 1	0 1 1	0 1 0
1 0 1	1 0 1	1 0 1	1 0 1	1 0 0
1 1 0	1 1 1	1 1 0	1 1 0	1 1 1

16. Which is the truth table for the NAND function?

Ⓐ			Ⓑ			Ⓒ			Ⓓ			Ⓔ		
A	B	Q	A	B	Q	A	B	Q	A	B	Q	A	B	Q
1	1	1	0	0	0	0	0	1	0	0	0	0	0	0
0	1	1	0	1	1	0	1	1	0	1	1	0	1	0
1	0	1	1	0	1	1	0	1	1	0	1	1	0	0
1	1	0	1	1	1	1	1	0	1	1	0	1	1	1

17. What is the clock input used for in those circuits that have one?

- Ⓐ To tell time,
- Ⓑ To determine when to change its state,
- Ⓒ To determine when to change its input,
- Ⓓ To disable the output,
- Ⓔ To store the demultiplexer output in the ALU

18. Which is the truth table for a full-adder?

Ⓐ				Ⓑ				Ⓒ				Ⓓ				Ⓔ							
A	B	Co	S	A	B	Ci	Co	S	A	B	Ci	Co	S	A	B	Ci	Co	S	A	B	Ci	Co	S
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
0	1	0	1	0	0	1	0	0	0	0	1	0	1	0	0	1	0	1	0	0	1	1	1
1	0	0	1	0	1	0	0	0	0	1	0	0	1	0	1	0	0	1	0	1	0	1	1
1	1	1	0	0	1	1	1	0	0	1	1	1	0	0	1	1	1	0	0	1	1	0	0
				1	0	0	0	1	1	0	0	0	1	1	0	0	0	1	1	0	0	1	1
				1	0	1	1	1	1	0	1	1	0	1	1	1	1	0	1	0	1	0	0
				1	1	0	1	1	1	1	0	1	0	1	1	1	1	0	1	1	0	0	0
				1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1

19. Which is the truth table for a half-adder?

Ⓐ				Ⓑ				Ⓒ				Ⓓ				Ⓔ							
A	B	Co	S	A	B	Ci	Co	S	A	B	Ci	Co	S	A	B	Ci	Co	S	A	B	Ci	Co	S
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
0	1	0	1	0	0	1	0	0	0	0	1	0	1	0	0	1	0	1	0	0	1	1	1
1	0	0	1	0	1	0	0	0	0	1	0	0	1	0	1	0	0	1	0	1	0	1	1
1	1	1	0	0	1	1	1	0	0	1	1	1	0	0	1	1	1	0	0	1	1	0	0
				1	0	0	0	1	1	0	0	0	1	1	0	0	0	1	1	0	0	1	1
				1	0	1	1	1	1	0	1	1	0	1	1	1	1	0	1	0	1	0	0
				1	1	0	1	1	1	1	0	1	0	1	1	1	1	0	1	1	0	0	0
				1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1

20. What is the LSB of the decimal number 1234?

- Ⓐ 0, Ⓑ 1, Ⓒ 2, Ⓓ 3, Ⓔ 4

21. What is the LSB of the decimal number 123?

- Ⓐ 0, Ⓑ 1, Ⓒ 2, Ⓓ 3, Ⓔ 4

22. What do the signals labeled I0-In do on a multiplexer?

- Ⓐ Data inputs, Ⓑ Data outputs, Ⓒ Address inputs, Ⓓ Address outputs, Ⓔ Clock signals

23. What are signals labeled A0-An called on a multiplexer?

- Ⓐ Data inputs, Ⓑ Data outputs, Ⓒ Address inputs, Ⓓ Address outputs, Ⓔ Clock signals

24. What do the signals labeled A0-An do on a multiplexer?
- ☐ A Select which output to enable,
 - ☒ B Select which input to propagate,
 - ☐ C Select which output to disable,
 - ☐ D Select which input to disable,
 - ☐ E Select which boolean function to perform
25. Which signals on a demultiplexer are its inputs?
- ☒ A A0-An
 - ☒ B I0-In
 - ☐ C Q0-Qn
 - ☐ D Both A and B
 - ☐ E Both A and C
26. Which signals on a demultiplexer are its outputs?
- ☐ A A0-An
 - ☐ B I0-In
 - ☒ C Q0-Qn
 - ☐ D Both A and B
 - ☐ E Both A and C
27. What do the signals labeled F0-Fn do on an ALU?
- ☐ A Select which output to enable,
 - ☐ B Select which input to propagate,
 - ☒ C Select which arithmetic operation to perform,
 - ☒ D Select which logical operation to perform,
 - ☐ E Both C and D
28. Which circuit can add these two binary numbers: 1101 1100
- ☐ A RS-latch,
 - ☐ B Demultiplexer,
 - ☒ C ALU,
 - ☐ D Full Adder,
 - ☐ E Half adder
29. How many full adders are needed to add two signed 8 bit numbers?
- ☐ A 1,
 - ☐ B 2,
 - ☒ C 4,
 - ☐ D 8,
 - ☐ E 16
30. What types of clocks are used for registers?
- ☐ A RS,
 - ☐ B Level,
 - ☒ C Edge,
 - ☐ D Boolean,
 - ☐ E GPS
31. What is an RS latch used for?
- ☐ A To reset the ALU,
 - ☒ B To store one bit,
 - ☐ C To store two bits,
 - ☐ D To generate the overflow status,
 - ☐ E To trigger the Multiplexer
32. What is a bus?
- ☐ A A register,
 - ☐ B To store one bit,
 - ☐ C To store two bits,
 - ☒ D A collection of related signals,
 - ☐ E A collection of unrelated signals
33. Which of the following is true?
- ☒ A High-level-sensitive latches will retain the input present during the falling edge of the enable signal,
 - ☒ B High-level-sensitive latches allow the output to change multiple times when the enable signal is high,
 - ☒ C Falling-edge-triggered latches retain the input when the clock changes from 1 to 0,
 - ☒ D All of the above
 - ☐ E None of the above

The following waveform includes, among other things, the signals of an RS latch whose output is labeled Q :

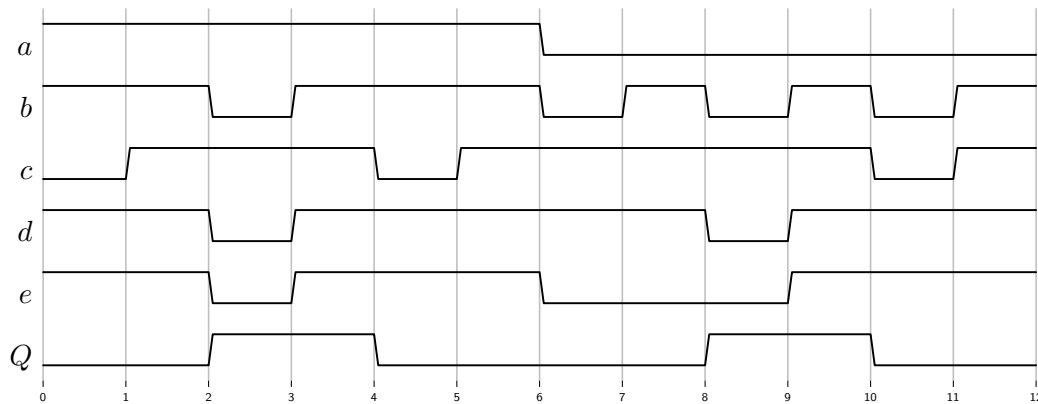


Figure 1: A Timing Diagram

34. Which signal labeled $a-e$ in Figure 1 is the *reset* signal? **c**
35. Which signal labeled $a-e$ in Figure 1 is the *set* signal? **d**
36. What does overflow mean?
 - A** A carry out of the LSB,
 - B** A carry into the MSB,
 - C** An operation can not fit into the destination register,
 - D** A logical operation has no inputs,
 - E** A collection of related signals
37. What signifies that an *unsigned* overflow has taken place during an addition?
 - A** A carry out of the LSB,
 - B** A carry into the MSB,
 - C** A carry out of the MSB,
 - D** A carry into the LSB that is is different from the carry out of the LSB,
 - E** A carry into the MSB that is is different from the carry out of the MSB
38. What signifies that a *signed* overflow has taken place during an addition?
 - A** A carry out of the LSB,
 - B** A carry into the MSB,
 - C** A carry out of the MSB,
 - D** A carry into the LSB that is is different from the carry out of the LSB,
 - E** A carry into the MSB that is is different from the carry out of the MSB
39. What the hexadecimal value of the binary number 10110001?
 - A** 69, **B** C0, **C** 19, **D** C2, **E** B1
40. What the hexadecimal value of the binary number 01101001?
 - A** 69, **B** C0, **C** 19, **D** C2, **E** B1
41. What the binary value of the hexadecimal number 22?
 - A** 10101010, **B** 11110000, **C** 00000000, **D** 10100101, **E** 00100010
42. What the binary value of the hexadecimal number A5?
 - A** 10101010, **B** 11110000, **C** 00000000, **D** 10100101, **E** 00100010

Given the following schematic symbol (that matches that discussed lecture), truth table and waveform diagram (labeled such that time t_0 appears at the far left edge and t_{16} appears at the right):

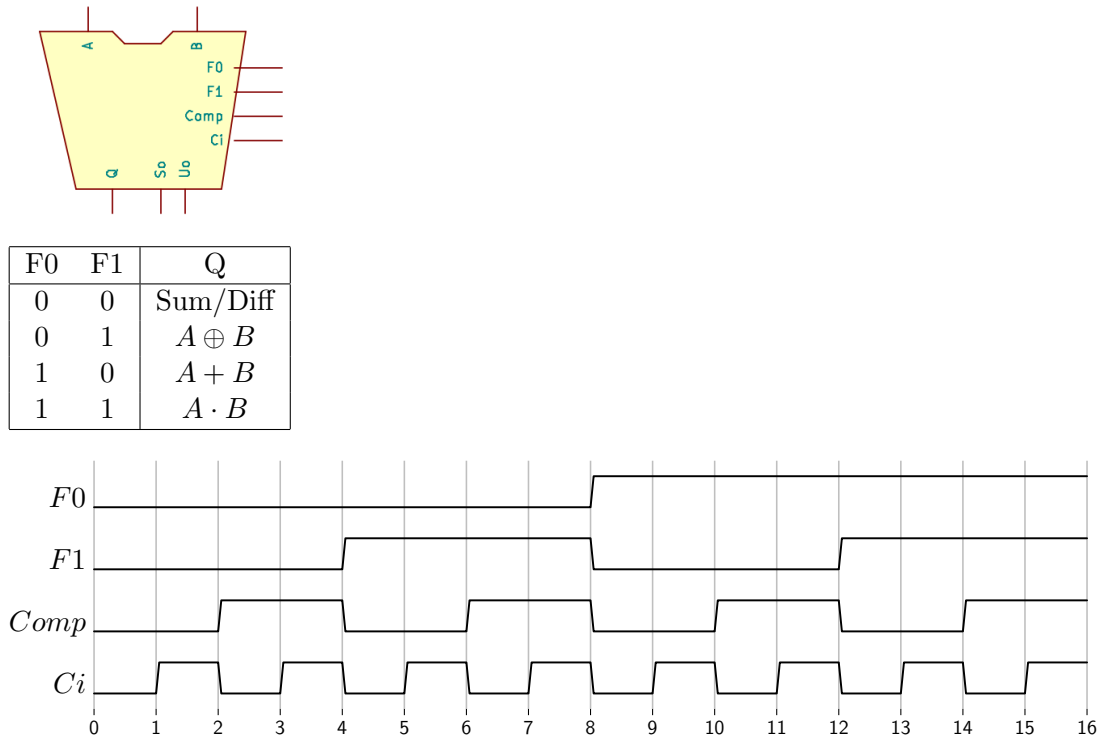


Figure 2: A Timing Diagram

43. What function is being performed between time t_0 and t_1 ?
☐ A Add, ☐ B Subtract, ☐ C XOR, ☐ D OR, ☐ E AND
44. What function is being performed between time t_3 and t_4 ?
☐ A Add, ☐ B Subtract, ☐ C XOR, ☐ D OR, ☐ E AND
45. What function is being performed between time t_4 and t_5 ?
☐ A Add, ☐ B Subtract, ☐ C XOR, ☐ D OR, ☐ E AND
46. What function is being performed between time t_8 and t_9 ?
☐ A Add, ☐ B Subtract, ☐ C XOR, ☐ D OR, ☐ E AND
47. What function is being performed between time t_{12} and t_{13} ?
☐ A Add, ☐ B Subtract, ☐ C XOR, ☐ D OR, ☐ E AND
48. What function is being performed between time t_{13} and t_{14} ?
☐ A Add, ☐ B Subtract, ☐ C XOR, ☐ D OR, ☐ E AND
49. What function is being performed between time t_5 and t_6 ?
☐ A $A \oplus B$, ☐ B $\bar{A} \cdot B$, ☐ C $A \cdot B$, ☐ D $A \cdot \bar{B}$, ☐ E $A + \bar{B}$
50. What function is being performed between time t_{14} and t_{15} ?
☐ A $A \oplus B$, ☐ B $\bar{A} \cdot B$, ☐ C $A \cdot B$, ☐ D $A \cdot \bar{B}$, ☐ E $A + \bar{B}$